

Electricity basics

- Electric charge
- Current
- Potential difference
- Resistance
- Ohm's law
- Series circuits
- Parallel circuits
- Combination circuits - series + parallel
- Power

Electric charge

- **Charge** is a fundamental property of matter.
- We are usually talking about the movement of electrons (negative charge).
- But in electrochemical process, there is also a movement of positive charged ions.
- **1 coulomb = The charge of 6.25×10^{18} electrons.**
- One electron has a charge of 1.60×10^{-19} coulombs.

Current

- Current is the measure of how much charge is moving through a point in a time period.
- A higher current means that more charge is moving.
- 1 amp = 1 coulomb / second (6.25×10^{18} electrons / second).
- Some scales: Nerve impulses - microamps, iPod - milliamps, toaster - amps, car engine starting - hundreds of amps, transmission lines, thousands of amps.
- A current of less than 100mA through the heart can be fatal.
- Electric current move slowly, but the electric field is nearly instant.

Low current - few electrons moving
High current - more electrons moving

Potential difference

- Separating positive & negative charge requires work to be done - this is a form of potential energy.
- A higher potential difference means that the charges carry more energy.
- This is the “push” behind electric charge. (Sometimes known as the Electro Motive Force - EMF)
- Measured in volts - 1 volt = 1 joule / coulomb

$$\text{Potential difference} = \frac{\text{Energy}}{\text{Charge}}$$

Potential differences can be positive or negative
- relative to the Earth at 0V.

Resistance

- Resistance is the measure of amount potential difference needs to be pushing to get an amp of current.
- Higher resistance: higher potential difference needed or lower current.
- 1 ohm = 1 volt / amp.
- We can consider a whole electric circuit to be the equivalent of one resistor.
- Adding resistors in series increases resistance.
- Adding resistors in parallel reduces resistance.

$$\text{Resistance} = \frac{\text{Potential difference}}{\text{Current}}$$



A 2500 Ω resistor (each colour indicates one of the numbers)

Ohm's law

Current can be increased in a circuit by:

- Increasing the potential difference pushes more electrons through.
- Decreasing the resistance to allow more electrons through.
- For example, a brighter globe has a lower resistance than a dim one.

$$\text{Current} = \frac{\text{Potential difference}}{\text{Resistance}}$$

$$I = \frac{V}{R}$$


An ohmic resistor has a constant resistance over a wide range of potential differences.

Series circuits

- The current through a series circuit is the same at all points.
- Around the whole circuit, the sum of the potential differences is zero.

$$R = R_1 + R_2 + \dots$$
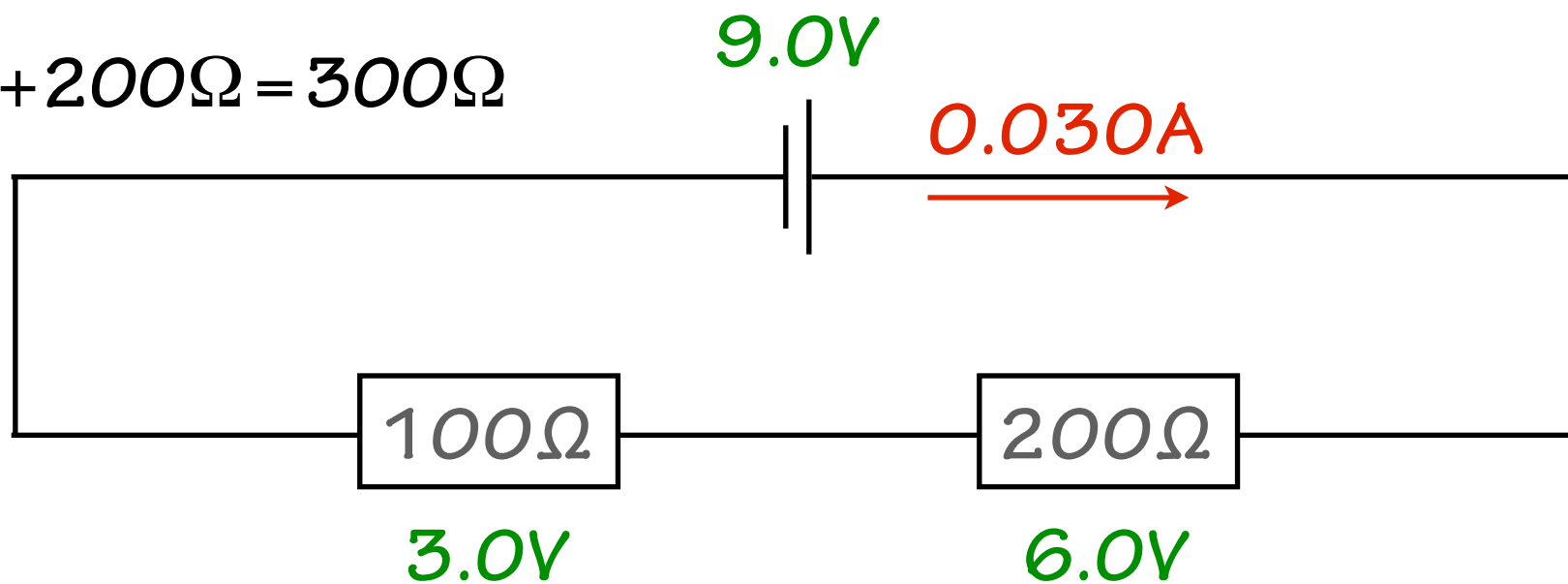
$$R = 100\Omega + 200\Omega = 300\Omega$$



$$I = \frac{V}{R}$$
$$I = \frac{9.0V}{300\Omega} = 0.030A$$

$$V = IR$$

$$V = 0.030A \times 100\Omega$$

$$V = 3.0V$$

$$V = 0.030A \times 200\Omega$$

$$V = 6.0V$$

This is also known as a **voltage divider** - the fraction of voltage is the as the fraction of resistance.

Parallel circuits


- The potential difference across two or more parallel components is the same.
- At any junction in the circuit, the sum of the currents in is equal to the sum of the currents out.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{100\Omega} + \frac{1}{200\Omega}$$

$$\frac{1}{R} = \frac{3}{200\Omega}$$

$$R = 67\Omega$$

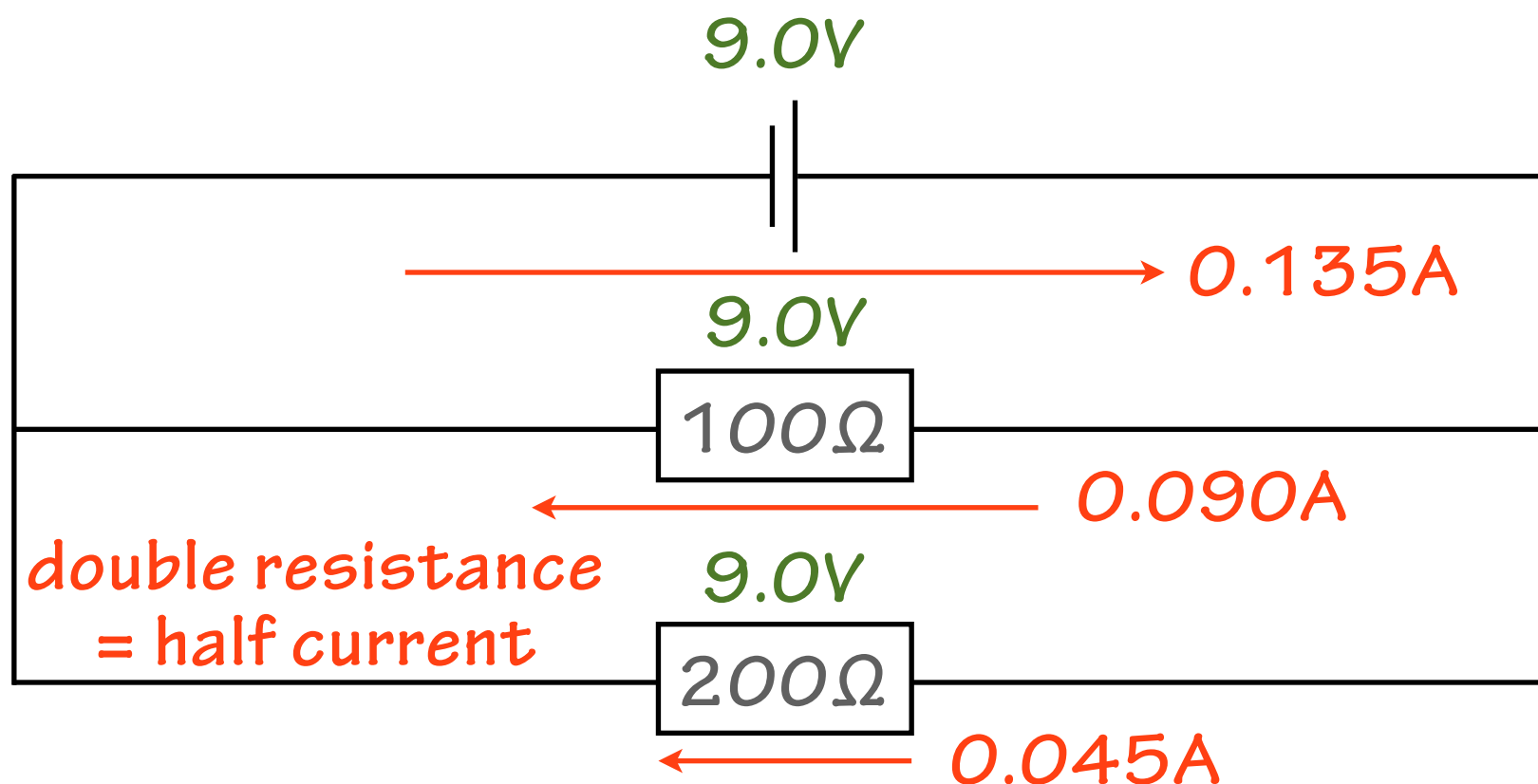

$$I = \frac{9.0V}{67\Omega} = 0.135A$$

$$I = \frac{9.0V}{100\Omega} = 0.090A$$

$$I = \frac{9.0V}{200\Omega} = 0.045A$$


Combination circuits - series + parallel

1. Find the total resistance.
2. Find the total current.
3. Use $I = V/R$ or resistance ratios for currents.
4. Use $V = IR$ or voltage divider rule for voltages.

$$V_1 = 0.0159\text{A} \times 500\Omega = 7.94\text{V}$$

$$V_2 = 9.00\text{V} \times \left(\frac{67\Omega}{567\Omega} \right) = 1.06\text{V}$$

$$V_3 = V_2 = 1.06\text{V}$$

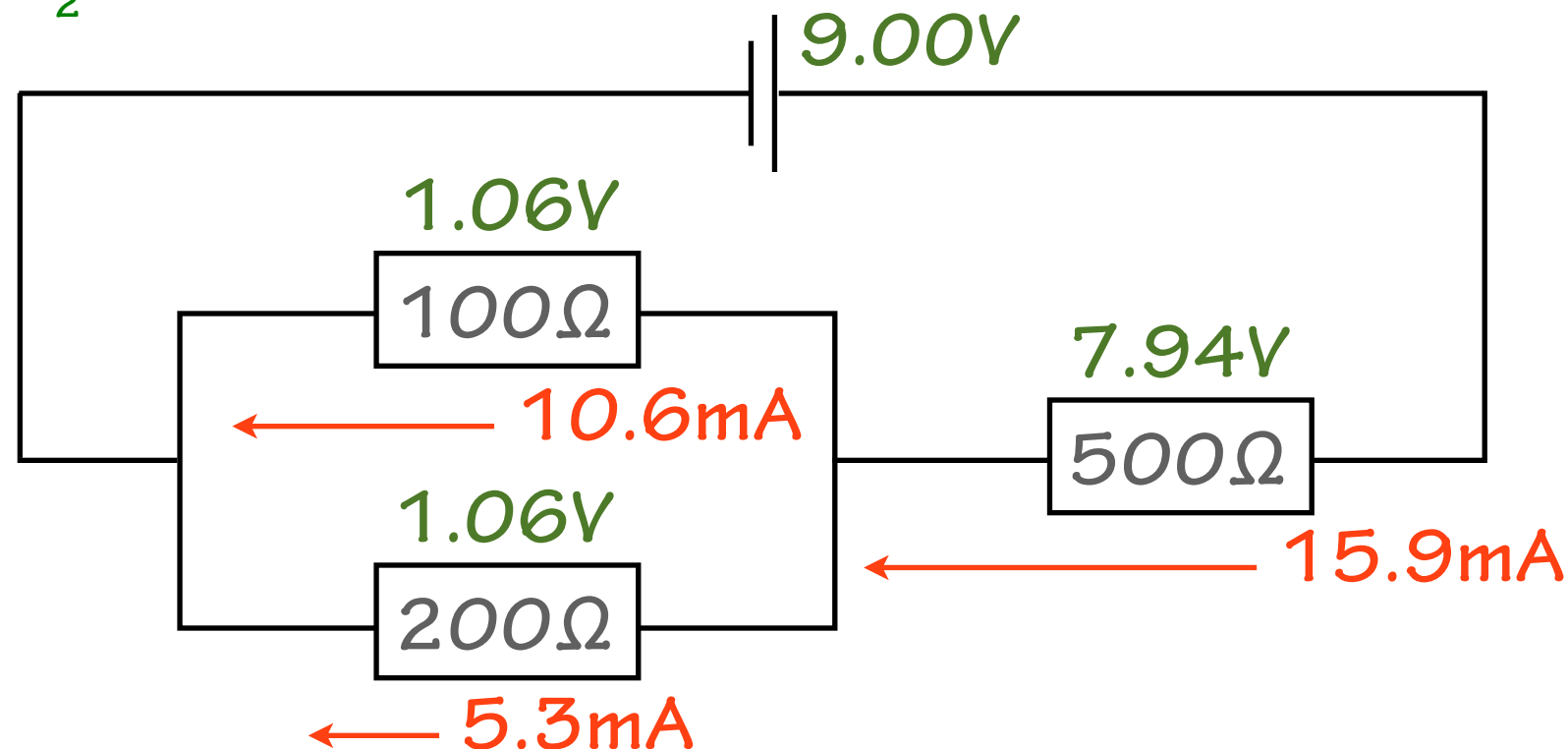

Parallel resistors

$$\frac{1}{R} = \frac{1}{100\Omega} + \frac{1}{200\Omega}$$

$$R = 67\Omega$$

Total resistance

$$R = 500\Omega + 67\Omega = 567\Omega$$

$$I_1 = \frac{9.00\text{V}}{567\Omega} = 0.0159\text{A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{1.06\text{V}}{100\Omega} = 0.0106\text{A}$$

$$I_3 = \frac{1}{3} \times 15.9\text{mA} = 5.3\text{mA}$$

Power

- Power is the measure of how much energy is dissipated through a device in a time period.
- 1 watt = 1 joule / second.

$$\frac{\text{Charge}}{\text{Time}} \times \frac{\text{Energy}}{\text{Charge}} = \frac{\text{Energy}}{\text{Time}}$$

$$P = \frac{E}{t} \longrightarrow E = Pt$$

$$P = IV$$

Power (Watts) →

Current (amps) →

Potential difference (volts) →

Some scales: torch light - watts, heater - kilowatts, electric generator - gigawatts.

Power calculations

- eg a light globe that draws a current of 200 mA at 240 V.
- $P = IV = 0.2A \times 240V = 48 W = 0.048 kW$
- Energy = Power x time = 0.048 kW x 24 hours
- In 24 hours, the total energy used is 1.15 kWh.
- This is the same as using 1.15 kW for 1 hour.
- Electricity is billed at around 20c per kWh.
- This would cost : 20c x 1.15 = 23 cents / day.
- Components in parallel - currents add, so does power.

$$1kWh = 3.6MJ$$