

# Electricity basics

---

- Electric charge
- Potential difference
- Current
- Resistance
- Ohm's law
- Series circuits
- Parallel circuits
- Combination circuits - series + parallel
- Power

# Electric charge

---

- **Charge** is a fundamental property of matter.
- We are usually talking about the movement of electrons (negative charge).
- But in electrochemical process, there is also a movement of positive charged ions.
- **1 coulomb = The charge of  $6.25 \times 10^{18}$  electrons.**
- One electron has a charge of  $1.60 \times 10^{-19}$  coulombs.

# Current

---

- Current is the measure of how much charge is moving through a point in a time period.
- A higher current means that more charge is moving.
- 1 amp = 1 coulomb / second ( $6.25 \times 10^{18}$  electrons / second).
- Some scales: Nerve impulses - microamps, iPod - milliamps, toaster - amps, car engine starting - hundreds of amps, transmission lines, thousands of amps.
- A current of less than 100mA through the heart can be fatal.
- Electric current move slowly, but the electric field is nearly instant.

---

---

Low current - few electrons moving  
High current - more electrons moving

# Potential difference

---

- Separating positive & negative charge requires work to be done - this is a form of potential energy.
- A higher potential difference means that the charges carry more energy.
- This is the “push” behind electric charge. (Sometimes known as the Electro Motive Force - EMF)
- Measured in volts - 1 volt = 1 Joule / coulomb

$$\text{Potential difference} = \frac{\text{Energy}}{\text{Charge}}$$

Potential differences can be positive or negative  
- relative to the Earth at 0V.

# Resistance

- Resistance is the measure of amount potential difference needs to be pushing to get an amp of current.
- Higher resistance: higher potential difference needed or lower current.
- 1 ohm = 1 volt / amp.
- We can consider a whole electric circuit to be the equivalent of one resistor.
- Adding resistors in series increases resistance.
- Adding resistors in parallel reduces resistance.

$$\text{Resistance} = \frac{\text{Potential difference}}{\text{Current}}$$



A 2500  $\Omega$  resistor (each colour indicates one of the numbers)

# Ohm's law

Current can be increased in a circuit by:

- Increasing the potential difference pushes more electrons through.
- Decreasing the resistance to allow more electrons through.
- For example, a brighter globe has a lower resistance than a dim one.

$$\text{Current} = \frac{\text{Potential difference}}{\text{Resistance}}$$

$$I = \frac{V}{R}$$


An ohmic resistor has a constant resistance over a wide range of potential differences.

# Series circuits

- The current through a series circuit is the same at all points.
- Around the whole circuit, the sum of the potential differences is zero.

$$R = R_1 + R_2 + \dots$$
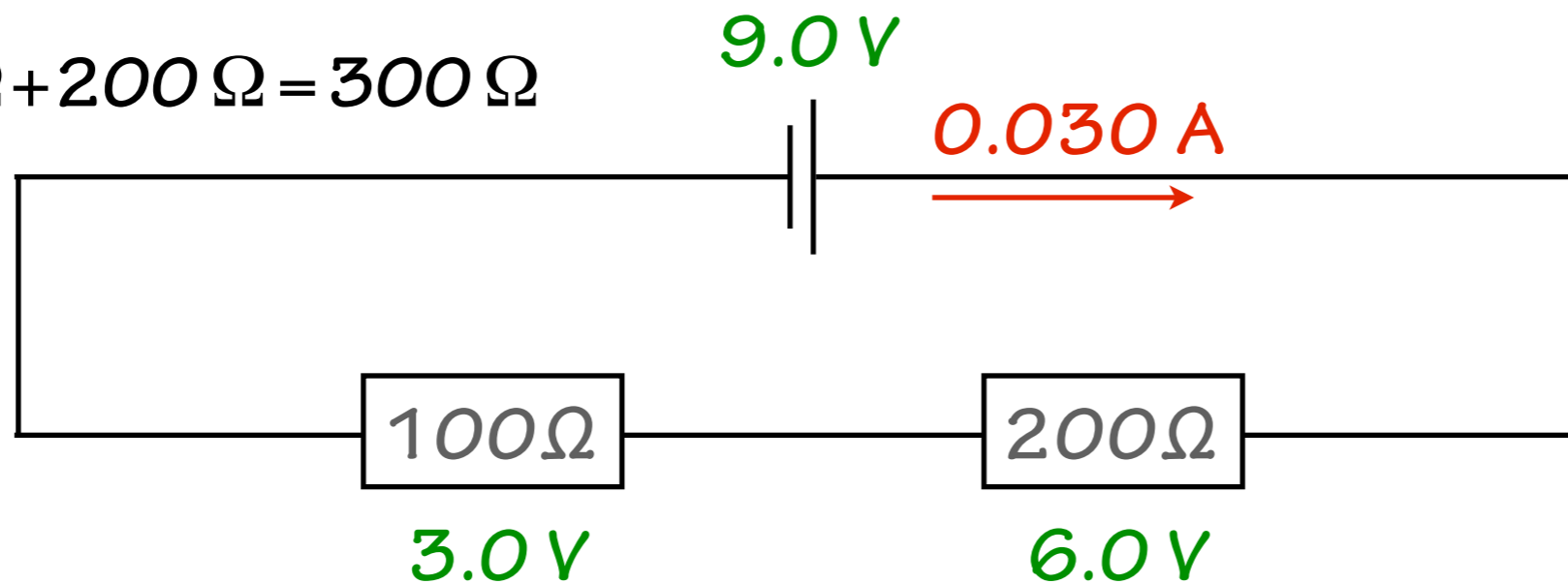
$$R = 100\ \Omega + 200\ \Omega = 300\ \Omega$$



$$I = \frac{V}{R}$$

$$I = \frac{9.0\text{ V}}{300\ \Omega} = 0.030\text{ A}$$

$$V = IR$$

$$V = 0.030\text{ A} \times 100\ \Omega$$

$$V = 3.0\text{ V}$$

$$V = 0.030\text{ A} \times 200\ \Omega$$

$$V = 6.0\text{ V}$$

This is also known as a **voltage divider** - the fraction of voltage is the as the fraction of resistance.

# Parallel circuits


- The potential difference across two or more parallel components is the same.
- At any junction in the circuit, the sum of the currents in is equal to the sum of the currents out.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{100\ \Omega} + \frac{1}{200\ \Omega}$$

$$\frac{1}{R} = \frac{3}{200\ \Omega}$$

$$R = 67\ \Omega$$

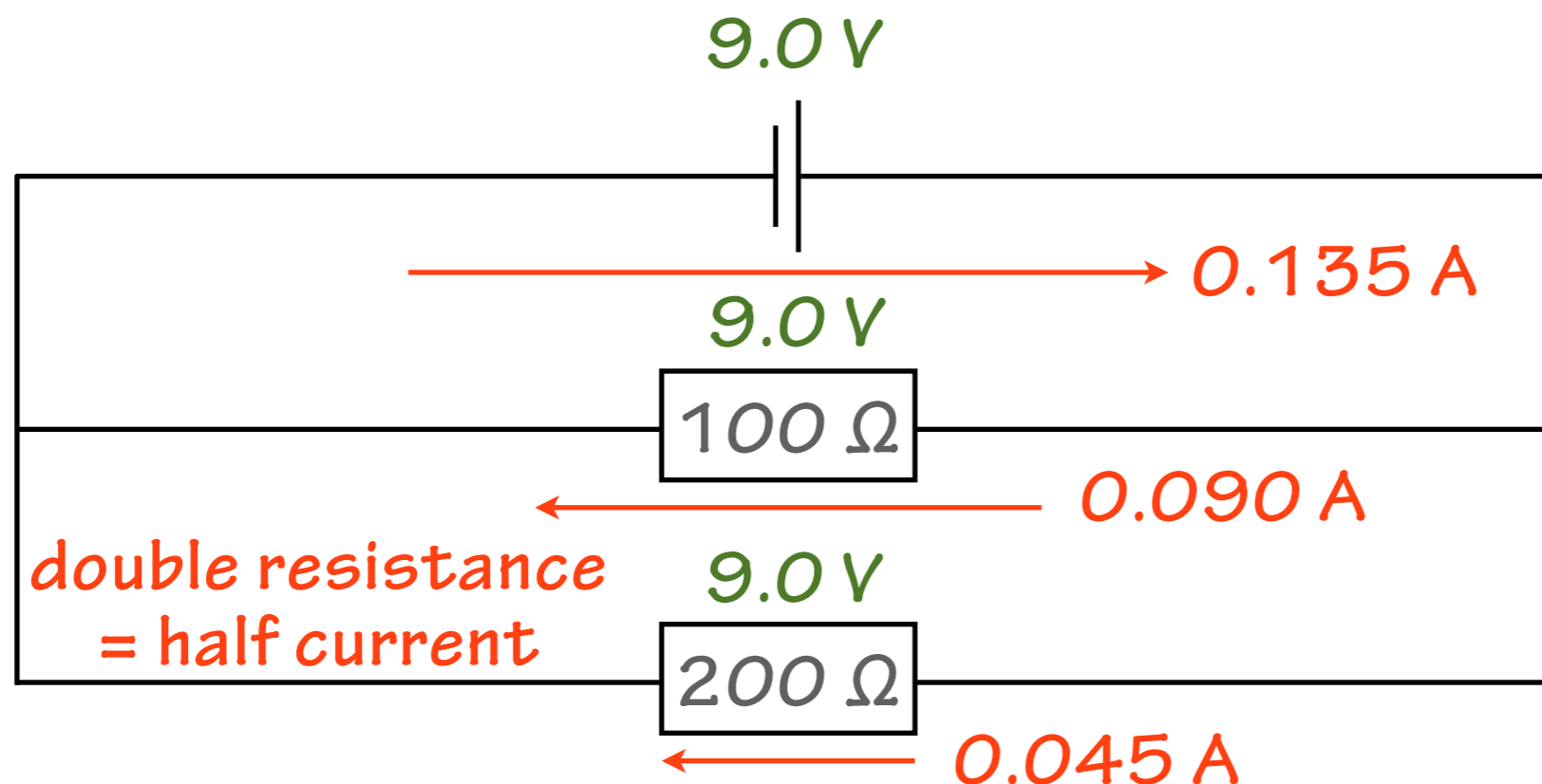

$$I = \frac{9.0\text{V}}{67\ \Omega} = 0.135\text{ A}$$

$$I = \frac{9.0\text{V}}{100\ \Omega} = 0.090\text{ A}$$

$$I = \frac{9.0\text{V}}{200\ \Omega} = 0.045\text{ A}$$




# Combination circuits - series + parallel

1. Find the total resistance.
2. Find the total current.
3. Use  $I = V/R$  or resistance ratios for currents.
4. Use  $V = IR$  or voltage divider rule for voltages.

$$V_1 = 0.0159 \text{ A} \times 500 \Omega = 7.94 \text{ V}$$

$$V_2 = 9.00 \text{ V} \times \left( \frac{67 \Omega}{567 \Omega} \right) = 1.06 \text{ V}$$

$$V_3 = V_2 = 1.06 \text{ V}$$

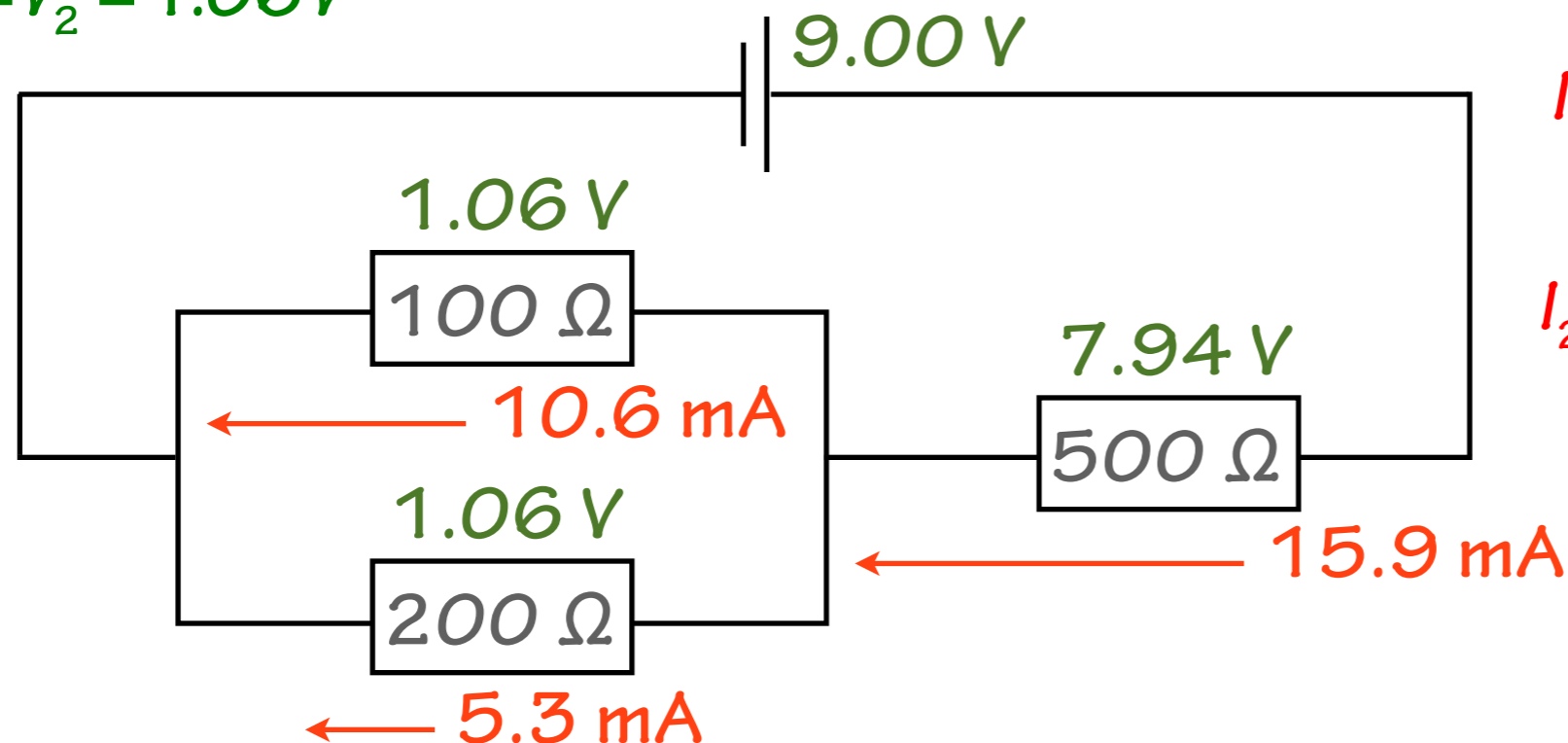

Parallel resistors

$$\frac{1}{R} = \frac{1}{100 \Omega} + \frac{1}{200 \Omega}$$

$$R = 67 \Omega$$

Total resistance

$$R = 500 \Omega + 67 \Omega = 567 \Omega$$

$$I_1 = \frac{9.00 \text{ V}}{567 \Omega} = 0.0159 \text{ A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{1.06 \text{ V}}{100 \Omega} = 0.0106 \text{ A}$$

$$I_3 = \frac{1}{3} \times 15.9 \text{ mA} = 5.3 \text{ mA}$$

# Power

- Power is the measure of how much energy is dissipated through a device in a time period.
- 1 Watt = 1 Joule / second.

$$\frac{\text{Charge}}{\text{Time}} \times \frac{\text{Energy}}{\text{Charge}} = \frac{\text{Energy}}{\text{Time}}$$

$$P = \frac{E}{t} \longrightarrow E = Pt$$

$$P = IV$$

The diagram shows the equation  $P = IV$  with three arrows pointing to the variables: a blue arrow from 'Power (Watts)' to 'P', a red arrow from 'Current (amps)' to 'I', and a green arrow from 'Potential difference (volts)' to 'V'.

Some scales: torch light - watts, heater - kilowatts, electric generator - gigawatts.

# Power calculations

- eg a light globe that draws a current of 200 mA at 240 V.
- $P = IV = 0.2A \times 240V = 48 W = 0.048 \text{ kW}$
- Energy = Power x time =  $0.048 \text{ kW} \times 24 \text{ hours}$
- In 24 hours, the total energy used is 1.15 kWh.
- This is the same as using 1.15 kW for 1 hour.
- Electricity is billed at around 25c per kWh.
- This would cost :  $25c \times 1.15 = 29 \text{ cents / day.}$

$$1 \text{ kWh} = 1000 \text{ J / s} \times 3600 \text{ s} = 3.6 \text{ MJ}$$